



CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15ELN15

First Semester B.E. Degree Examination, Dec.2015/Jan.2016 Basic Electronics


Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

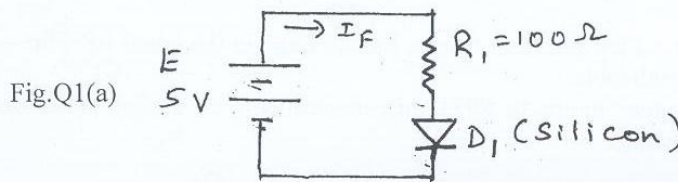- 1 a. For the circuit shown in fig.Q1(a) draw the DC load line and locate Q – pt. (04 Marks)



- b. What is the need for capacitor filter? For a Half – Wave Rectifier, explain the operation of C – filter. (06 Marks)
- c. Considering npn transistor in common emitter configuration, explain how it acts as voltage amplifier. (06 Marks)

OR

- 2 a. Explain the working of a Bridge Full – Wave Rectifier, with a neat circuit diagram and waveforms. (06 Marks)
- b. Discuss the load and line regulation using zener diode with neat circuit diagram and appropriate expressions. (06 Marks)
- c. Calculate the values of I_C and I_E for a BJT with $\alpha_{dc} = 0.97$ and $I_B = 50 \mu A$. Determine β_{dc} . (04 Marks)

Module-2

- 3 a. Precisely analyse the circuit of voltage divider bias and hence determine the V_C and V_{CE} . Mention the advantages of voltage divider bias. (10 Marks)
- b. Derive an equation for output voltage for a non – inverting Op – amp. Find the gain of amplifier if $R_F = 10K\Omega$ and $R_1 = 1K\Omega$. (06 Marks)

OR

- 4 a. A base bias circuit with a 12V supply uses a transistor with $h_{FE} = 70$. Design the circuit so that $I_C = 2mA$ and $V_{CE} = 9V$ (Assume $R_E = 0$). (06 Marks)
- b. Explain the working of Op – amp as integrator. (05 Marks)
- c. Derive the expression of 3 input summing amplifiers. (05 Marks)

Module-3

- 5 a. Convert the following : i) $172.625_{(10)} = ()_2$ ii) $(ABCD.72)_{16} = ()_8$
iii) $(10111101.0101)_2 = ()_{10}$. (06 Marks)
- b. Perform the following operations using 1's and 2's compliment technique
i) $(56)_{10} - (79)_{10}$ ii) $(23)_{10} - (18)_{10}$. (06 Marks)
- c. State and prove de Morgan's theorem using truth table for 2 variables. (04 Marks)

Important Note : 1. On completing your answers, carefully draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appraised to evaluator, will be treated as malpractice.

OR

- 6 a. Explain full adder circuit with truth table. Realise the circuit for sum and carry using basic gates. Also write the diagram showing FA using two half adders. (06 Marks)
- b. Simplify and realize the following expressions using only NAND and NOR.
- i) $Y = (A + \bar{B})(B + C)(\bar{C} + \bar{B})$ ii) $Y = AB + AC + BD + CD.$ (10 Marks)

Module-4

- 7 a. Explain the operation of NOR Latch with symbol, circuit and truth table. (06 Marks)
- b. With a neat block diagram, explain the architecture of 8051 microcontroller. (10 Marks)

OR

- 8 a. How is Flip – Flop different from a Latch? Explain the gated RS Flip – Flop with symbol, circuit and truth table. (08 Marks)
- b. Interface stepper motor to 8051 microcontroller with a neat block diagram. Explain its working principle. (08 Marks)

Module-5

- 9 a. Explain Amplitude Modulation with relevant waveforms. Derive the equation for instantaneous value of modulated signal in volts and define modulation index. (08 Marks)
- b. Define the term transducer. Mention any four characteristics a transducer should possess. (02 Marks)
- c. Briefly explain the working of thermistor. Mention its applications. (06 Marks)

OR

- 10 a. Explain the frequency modulation with necessary waveforms. Bring out the difference between AM and FM. (08 Marks)
- b. Explain construction and the principle of operation of LVDT. (08 Marks)

* * * * *



USN ISPI4ME040

14ELN15/25

First/Second Semester B.E. Degree Examination, Dec.2015 / Jan.2016

Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting ONE full question from each module.

Module - 1

- 1 a. Draw and explain the V-I characteristics of a silicon diode. (08 Marks)
- b. What is a rectifier? With a neat circuit diagram and waveforms, explain the working of full wave rectifier. (08 Marks)
- c. A full wave rectifier with a load of 1 KΩ. The ac voltage applied to the diode is 200-0-200 V, if diode resistance is neglected. Calculate:
 - i) Average dc current;
 - ii) Average dc voltage. (04 Marks)
- 2 a. Draw and explain the input and output characteristics of common emitter configuration. (08 Marks)
- b. Explain full wave rectifier with capacitor filter with necessary waveforms. (07 Marks)
- c. In common emitter transistor circuit if $\beta = 100$ and $I_B = 50 \mu A$, compute the values of I_C , I_E and α . (05 Marks)

Module - 2

- 3 a. With a neat circuit diagram, explain the voltage divider bias circuit by giving its exact analysis. (08 Marks)
- b. For the base bias circuit for npn transistor, find I_B , I_C and V_{CE} if $R_C = 2.2 K\Omega$, $R_B = 470 K\Omega$, $V_{CC} = 18 V$, $h_{fe} = 100$. Draw the dc load line and Q point. (08 Marks)
- c. What is op-amp? List the ideal characteristics of an op-amp. (04 Marks)
- 4 a. Define for an op-amp (i) CMRR, (ii) Slew rate, (iii) PSRR. (06 Marks)
- b. Show how an op-amp can be used as integrator. Derive an expression for its output. (06 Marks)
- c. For the circuit shown in Fig.Q4(c). Calculate the output voltage.

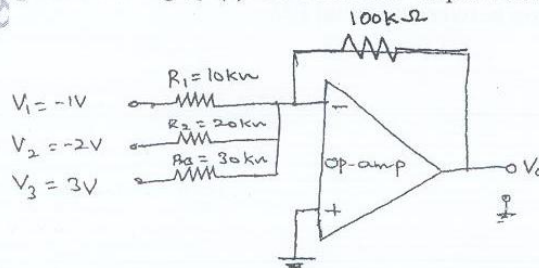


Fig.Q4(c)

- d. What is voltage follower? Explain. (04 Marks)

Module - 3

- 5 a. Convert :
 - i) $(35.45)_{10} = ()_2$
 - ii) $(475.25)_8 = ()_{10}$
 - iii) $(3FD)_{16} = ()_2$

(06 Marks)

Important Note : 1. On completing your answers, computerily draw diagonal cross lines on the remaining blank page. 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- b. State and prove Demorgan's theorems. (06 Marks)
- c. Show that:
- i) $\overline{ABC} + B + \overline{BD} + \overline{ABD} + \overline{AC} = B + C$
- ii) $\overline{AB} + \overline{A} + AB = 0$
- iii) $AB + A(B + C) + B(B + C) = B + AC$ (06 Marks)
- d. What are universal gates? (02 Marks)
- 6 a. Realize two input EX-OR gate using only NAND gates. (05 Marks)
- b. Design full adder and implement it. (07 Marks)
- c. Subtract $(111001)_2$ from $(101011)_2$ using 2's complement method. (04 Marks)
- d. Realize OR gate using diodes and explain. (04 Marks)

Module – 4

- 7 a. Define flip flop. Explain R-S flip flop. (05 Marks)
- b. With neat block diagram, explain architecture of 8085 microprocessor. (10 Marks)
- c. List the difference between microprocessor and microcontroller. (05 Marks)
- 8 a. What is transducer? Distinguish between active and passive transducer. (05 Marks)
- b. With a neat sketch, explain construction and working of LVDT. (07 Marks)
- c. Explain the working of photo voltaic transducer. (08 Marks)

Module – 5

- 9 a. What is modulation? What is the need of modulation? (05 Marks)
- b. A 500 W, 1 MHz carrier is amplitude modulated with a sinusoidal signal of 1 kHz. The depth of modulation is 60%. Calculate the bandwidth, power in the sidebands and the total power transmitted. (07 Marks)
- c. Define AM. Draw the AM signal and its spectrum. Derive the necessary expressions for AM. (08 Marks)
- 10 a. With a block diagram, explain typical cellular mobile unit. (05 Marks)
- b. What is ISDN? Explain services of ISDN. (06 Marks)
- c. Explain advantages and applications of optical fibers. (05 Marks)
- d. Give the comparison between AM and FM. (04 Marks)

* * * * *